5.7.2 Parallel Circuit

In a parallel circuit, there is more than one resistor (bulb) and they are arranged on many paths. This means charges (electrons) can travel from one end of the cell through many branches to the other end of the cell. Here, voltage across the resistors (bulbs) remains the same but the current flowing through the circuit gets divided across each resistor.

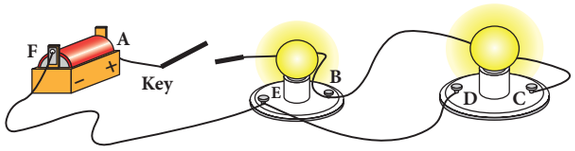


Figure 5.15 Parallel circuit

In the above diagram, current can flow in two paths: ABEFA and ABCDEFA. Here, it is clear that electricity from the cell can take either path ABEFA or path ABCDEFA to return to the cell. From the diagram you will notice that even when one resistor (bulb) burns out, the other bulbs will work because the electricity is not flowing through only one path. All the light bulbs in our homes are connected in parallel circuit. If one bulb burns out, the other bulbs in the rooms will still work. The bulbs in a parallel circuit do not dim out as in series circuits. This is because the voltage across one branch is the same as the voltage across all other branches.

Let us consider three bulbs connected in series. Let V be the voltage across the bulbs and I_1, I_2, I_3 be the current across each bulb. The current I from the battery is the total of the individual current flowing through the resistances (bulbs).

$$I = I_1 + I_2 + I_3$$

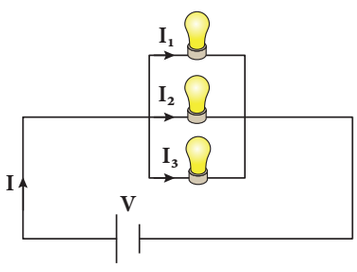


Figure 5.16 Current in parallel circuit

Table 5.1 Difference between series and parallel circuits

Series circuit	Parallel circuit
Same amount of current flows through all the components.	The current flowing through each component combines to form the current flow.
Voltage is different across different components.	Sum of the through each component will be the voltage drawn from the source.
Components are arranged in a line.	Components are arranged parallel to each other.
If one component breaks down, the whole circuit will burn out.	Other components will function even if one component breaks down.


5.8 Effects of Current

When current is flowing through a conductor it produces certain effects. These are known as effects of electric current. These effects result in conversion of electrical energy into different forms of energies such as heat energy, mechanical energy, magnetic energy, chemical energy and so on.

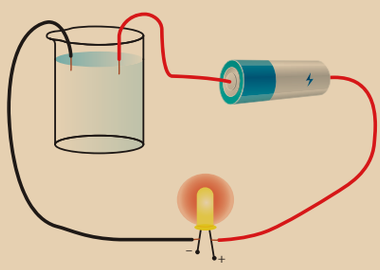5.8.1 Chemical effect of current

Activity 5

Take two pieces of wire, an LED light and a battery, and make a simple electric circuit. Take some water in a glass and put the wires in the water as shown in the figure. Does the LED bulb glow? What do you understand from this?



8th_Science_Unit-5_EM.indd 54 12/1/2022 3:24:57 PM